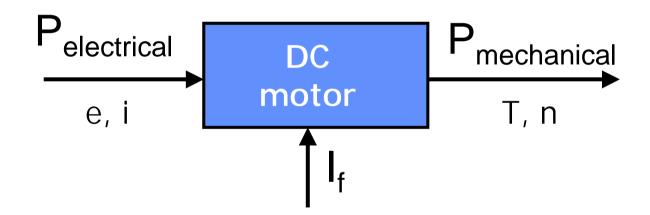




## Hour 6









# Torque Equation (Sect. 4.2.5)

- Equation 4.17a:  $E_a I_a = T \omega_m$
- Equation 4.17:  $T = K_a \Phi I_a$ (where  $K_a = Np/\pi a$ or  $K_a = Zp/2\pi a$ )
- Example 4.1 (P.139)




## Speed Equation

Since 
$$E_a = K_a \Phi \omega_m = V_t - I_a R_a$$
,  
then re-arrange:

$$\omega_{\rm m} = \frac{V_{\rm t} - I_{\rm a}R_{\rm a}}{K_{\rm a}\Phi}$$



## Separately Excited Motor (P.173)

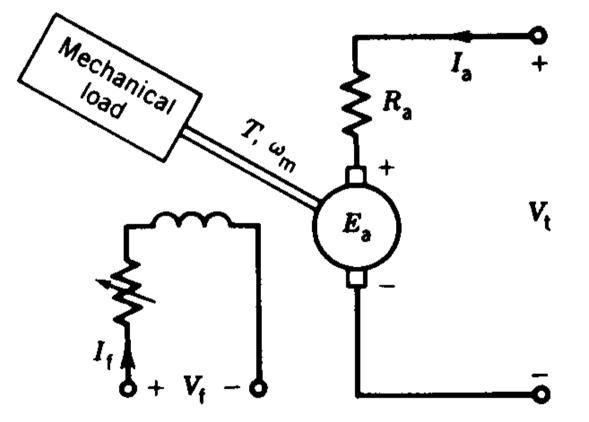



## Separately Excited Motor (P.173)


• From the circuit (Fig. 4.50)

$$V_{t} = E_{a} + IaR_{a}$$
$$E_{a} = V_{t} - I_{a}R_{a}$$
$$= K_{a}\Phi\omega_{m}$$

-  ${\rm I_a} \, and \, \omega_m$  depend on the mechanical load connected to the motor shaft




### Torque-speed Characteristic of Separately Excited Motor (Fig.4.51)

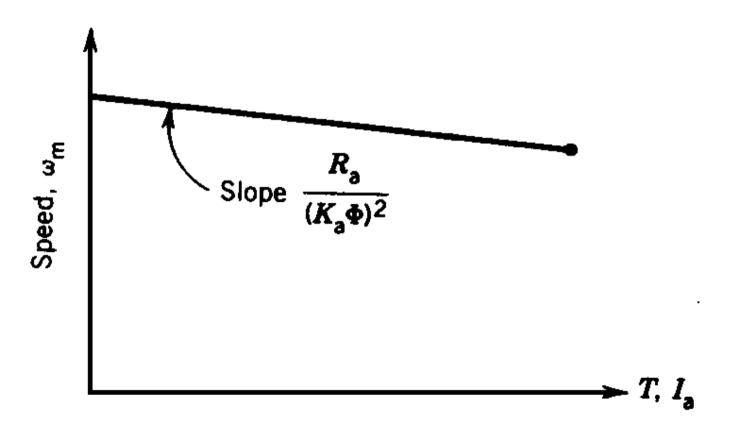





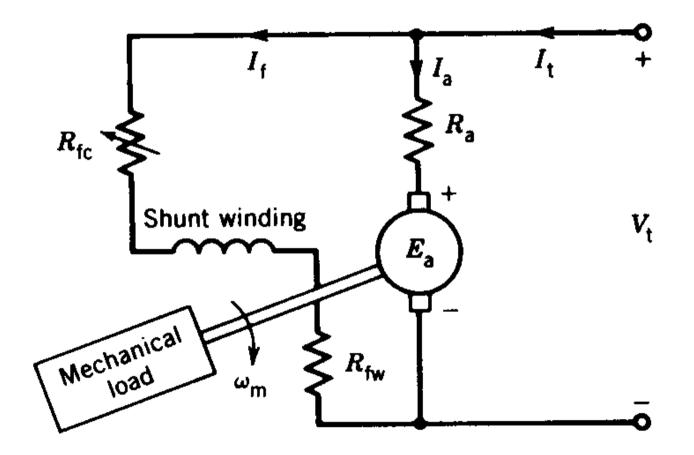

slide 8





- From the circuit (Fig. 4.48)  $V_a = E_a + I_a R_a$   $I_t = I_a + I_f$   $E_a = V_t - I_a R_a$  $= K_a \Phi \omega_m$
- $I_a$  and  $\omega_m$  depend on the mechanical load connected to the motor shaft
- Example 4.6 (P.170)



#### Torque-speed Characteristic of Shunt Motor

 Torque-speed Characteristic of a Shunt Motor is very similar to a Separately Excited Motor






Reading: sect. 4.4.2

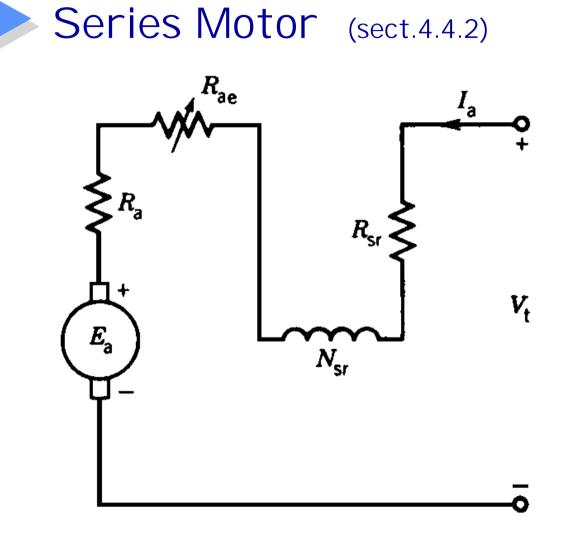
- **Circuit** (Fig. 4.55)
- Torque-speed Characteristic (Figure 4.55b)
- Example 4.9






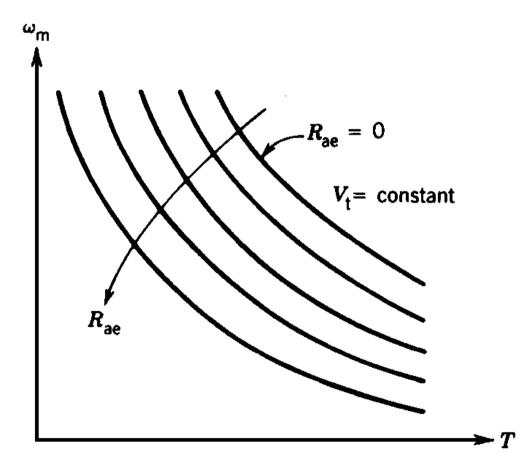
#### Torque-speed Characteristic of Series Motor (Fig.4.55b)





#### **Torque-speed Characteristics of Different DC Motors** (Fig. 4.56)

